

Microarchitecture

University of South Carolina

Introduction to Computer Architecture

Fall, 2024

Mehdi Yaghouti



**Molinaroli College of
Engineering and Computing**




UNIVERSITY OF SOUTH CAROLINA

Microarchitecture

- A computer architecture is defined by its instruction set and architectural state
- RISC-V architectural state: the program counter and the 32 X 32-bit registers
- Architectural state and memory hold all the needed information to resume
- Microarchitecture is the connection between logic and architecture
- Microarchitecture is the arrangement of:
 - Registers
 - Arithmetic Logic Units (ALUs)
 - Finite State Machines (FSMs)
 - Memories
 - Logic building blocksneeded to implement a specific architecture
- Microarchitecture can be considered to be composed of *datapath* and *control unit*
 - *datapath* is the path in which the data flow between different components
 - *control unit* controls the datapath based on the current instruction at hand



Main Components

- Program counter (PC) points to the current instruction
- PCNext, indicates the address of the next instruction
- Instruction memory takes a 32-bit address A and reads the data
- Register file has two read ports and one write port
- Read ports take 5-bit address inputs, A1 and A2
- Register file places the 32-bit register values onto RD1 and RD2
- It takes a 5-bit address input A3 and a 32-bit write data WD3
- If WE3 is asserted, the data WD3 will be written into address A3
- Writing happens at the clock edge
- Data memory has a single read/write port
- It reads data at address A and places it into RD
- If WE is asserted it writes WD into address A at the clock edge

   


Fetch

  - PC is the current instruction address
- Each word is 32 bits
- $PCNext \leftarrow PC + 4$
- PC only changes at the clock transition
- Branch instructions need to set the $PCNext$




Bitfield Extraction

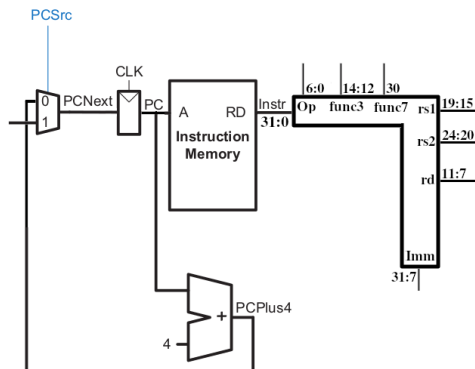- *PC* is the current instruction address



Registers

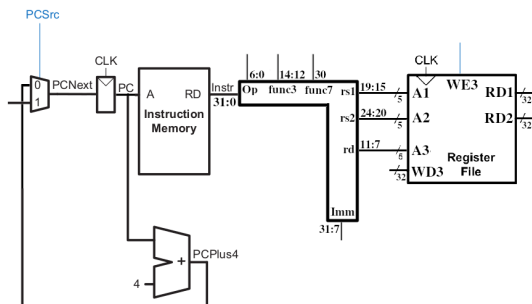- *PC* is the current instruction address



Extension Unit


- PC is the current instruction address

ImmSrc	ImmExt	Type	Description
00	{{20{Instr[31]}}, Instr[31:20]}	I	12-bit signed immediate
01	{{20{Instr[31]}}, Instr[31:25], Instr[11:7]}	S	12-bit signed immediate
10	{{20{Instr[31]}}, Instr[7], Instr[30:25], Instr[11:8], 1'b0}	B	13-bit signed immediate
11	{{12{Instr[31]}}, Instr[19:12], Instr[20], Instr[30:21], 1'b0}	J	21-bit signed immediate




Sign Extension

- PC is the current instruction address

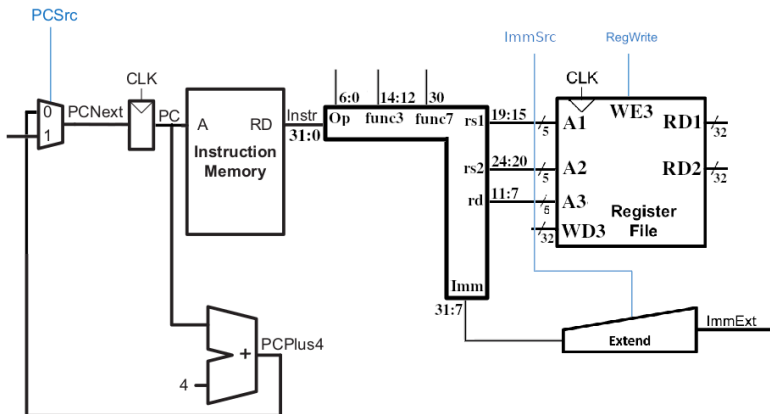

ALU


- PC is the current instruction address

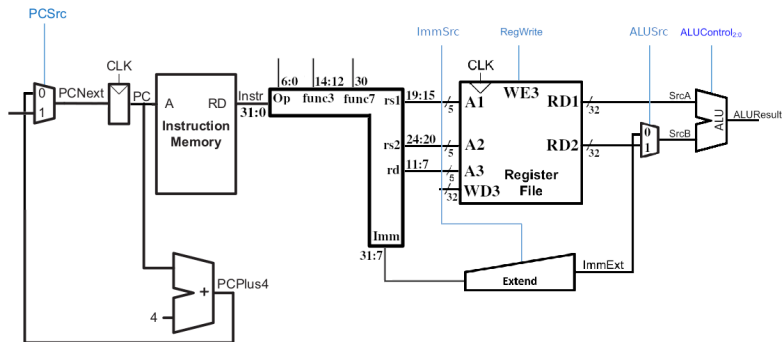

Load Instruction

• `lw rd, imm(rs1)`

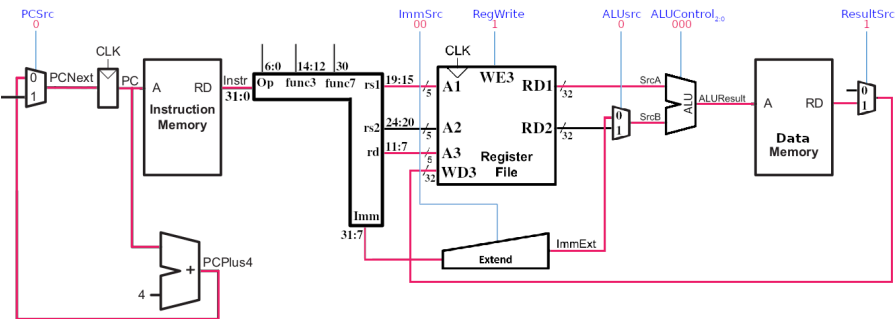
- 1 Read one source register
- 2 Perform addition with immediate
- 3 Write the second source register into data memory



Store Instruction

• `sw rs2, imm(rs1)`

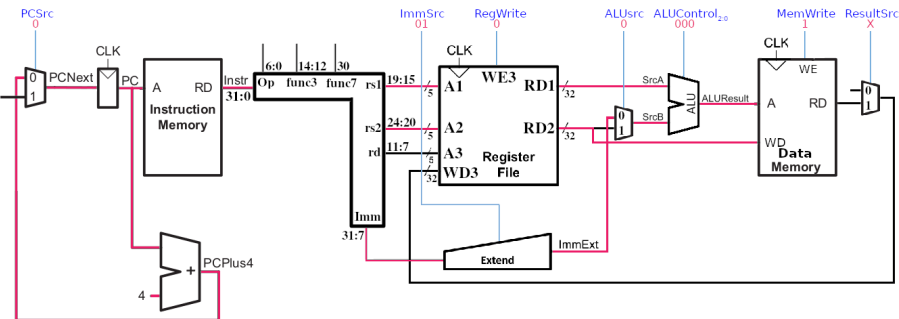
- 1 Read two source registers
- 2 Perform addition between a source register and immediate
- 3 Write the second source register into the memory



R-Type Instruction

- add, sub, and, or, slt
- They only differ in ALUControl
- add rd, rs1, rs2,
 - 1 Read two source registers
 - 2 Perform ALU operation
 - 3 Write back the ALU result into destination register


ALUControl _{2,0}	Function
000	Add
001	Subtract
010	AND
011	OR
101	SLT

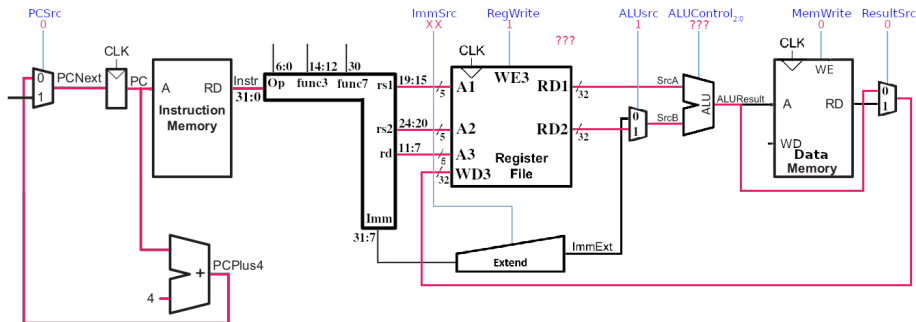

I-Type Instruction


- `addi, andi, ori, slti`
- They only differ in `ALUControl`
- `addi rd, rs1, imm,`
 - 1 Read one source register
 - 2 Perform ALU operation between the source and `Imm`
 - 3 Write back the ALU result into destination register

<code>ALUControl_{2,0}</code>	Function
000	Add
001	Subtract
010	AND
011	OR
101	SLT

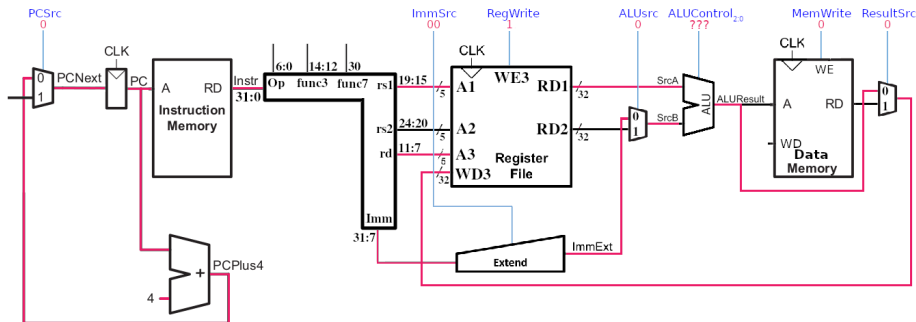

Conditional Branch

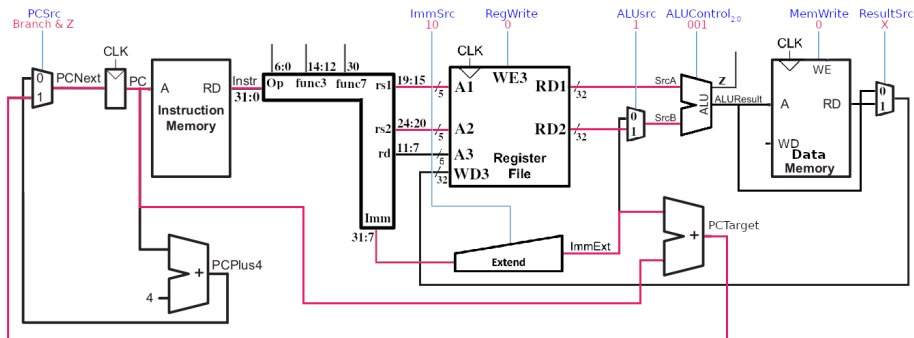
- `beq rs1, rs2, addr,`
 - 1 Read two source registers
 - 2 Perform the subtraction and issue Z
 - 3 Calculate $PC+Imm$
 - 4 Choose the select signal for $PCSrc$



Jump Instruction


• `jal rd, label,`

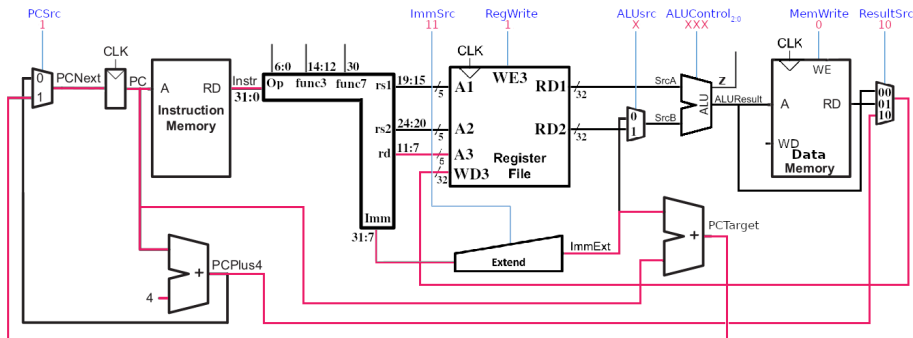- ① Jump to $Pc+imm$
- ② Write $Pc+4$ into `rd`



Control Unit

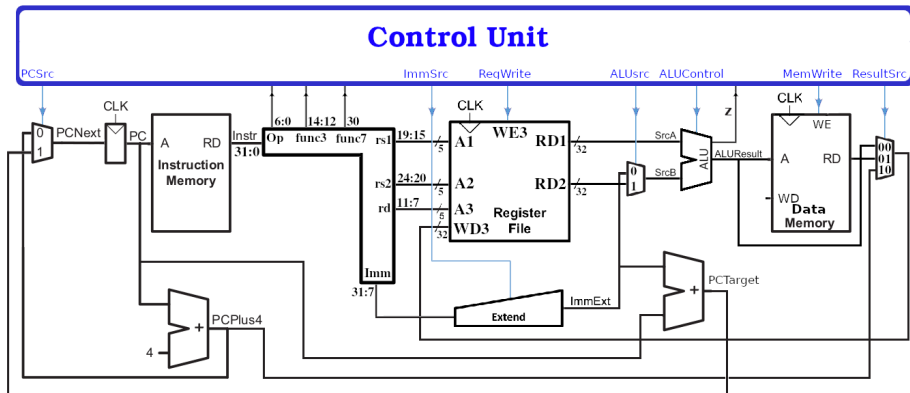
- Op (6:0), func3 (14:12) and func7 (30) are the inputs to the control unit
- Outputs: PCSrc, ImmSrc, RegWrite, ALUSrc, ALUControl, MemWrite, ResultSrc



Control Unit


Instruction	Opcode	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
lw	0000011	1	00	1	0	01	0	00	0
sw	0100011	0	01	1	1	xx	0	00	0
R-type	0110011	1	xx	0	0	00	0	10	0
beq	1100011	0	10	0	0	xx	1	01	0
I-type ALU	0010011	1	00	1	0	00	0	10	0
jal	1101111	1	11	x	0	10	0	xx	1

• Main Decoder truth tabel

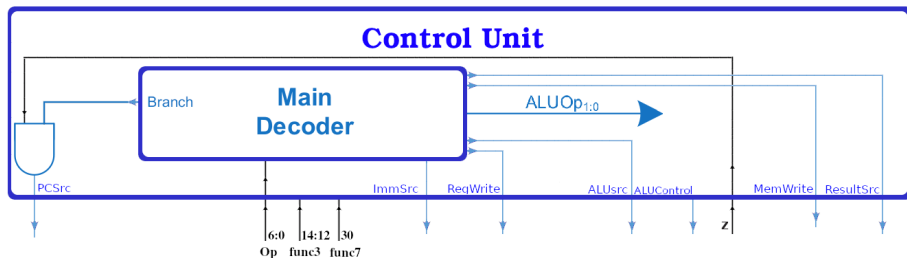

ALUOp	funct3	[op _s , funct7 _s]	ALUControl	Instruction
00	x	x	000 (add)	lw, sw
01	x	x	001 (subtract)	beq
10	000	00, 01, 10	000 (add)	add
	000	11	001 (subtract)	sub
	010	x	101 (set less than)	slt
	110	x	011 (or)	or
	111	x	010 (and)	and

- ALU truth tabel

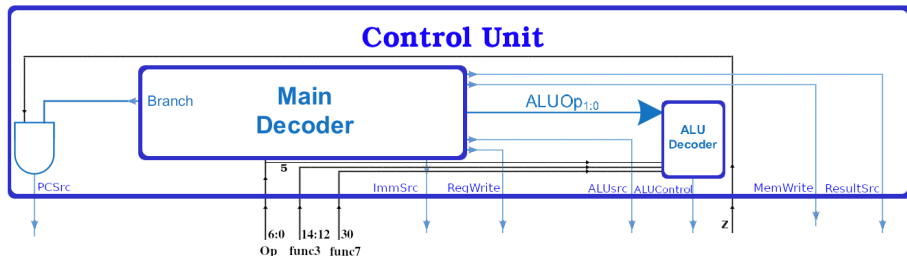

Performance Analysis

- The CPU performance


$$ExecutionTime = (\#Inst.) \times (CPI) \times \frac{1}{F_{clock}}$$

- In single cycle CPU, $CPI=1$
- The cycle time is set by the critical path
- lw has the longest path

$$T_{single} = t_{pcq} + t_{mem} + \max\{t_{RRead}, t_{dec} + t_{ext} + t_{mux}\} + t_{ALU} + t_{mem} + t_{mux} + t_{RSetup}$$

- Assuming that $t_{RRead} > t_{dec} + t_{ext} + t_{mux}$,
 
$$T_{single} = t_{pcq} + 2t_{mem} + t_{RRead} + t_{ALU} + t_{mux} + t_{RSetup}$$



Performance Analysis

- Using the following table, the clock cycle can be estimated as

$$T_{single} = t_{pcq} + 2t_{mem} + t_{RFread} + t_{ALU} + t_{mux} + t_{RFsetup}$$

$$= 40 + 2 \times 200 + 100 + 120 + 30 + 60 = 750ps$$


Element	Parameter	Delay (ps)
Register clk-to-Q	t_{pcq}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	30
AND-OR gate	t_{AND-OR}	20
ALU	t_{ALU}	120
Decoder (control unit)	t_{dec}	25
Extend unit	t_{ext}	35
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

Disadvantages

- Requires a clock cycle long enough to support the slowest instruction
- Requires separate memories for instructions and data
- Hardware are not being used efficiently, e.g. one adder for each task


Combining the Memories

 - Instruction and Data memories can be unified using a multiplexer for the address




Combining the Memories

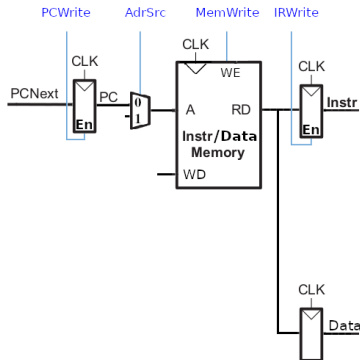- Instruction and Data memories can be unified using a multiplexer for the address
- The Instruction and data need to be stored in registers




Instruction Decoding

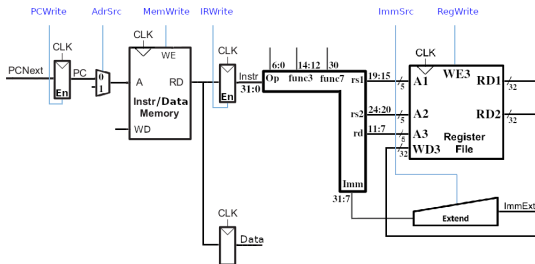- Instruction and Data memories can be unified using a multiplexer for the address
- The Instruction and data need to be stored in registers
- Instructions are the same as before, so is the instruction decoder!



ALU

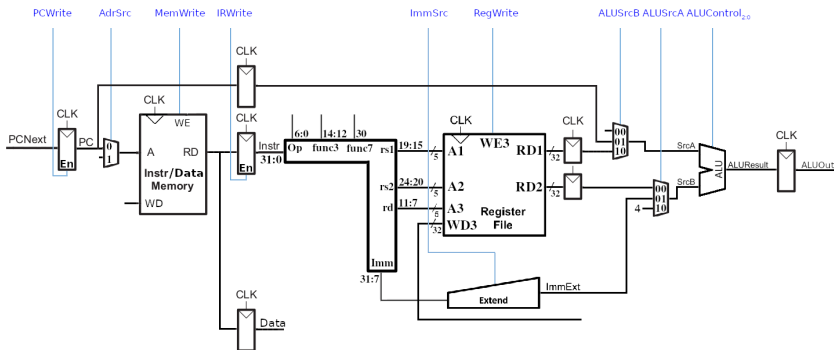- Instruction and Data memories can be unified using a multiplexer for the address
- The Instruction and data need to be stored in registers
- Instructions are the same as before, so is the instruction decoder!
- We can save adders by reusing ALU for all the additions



Big Problem


- Instruction and Data memories can be unified using a multiplexer for the address
- The Instruction and data need to be stored in registers
- Since the instructions are the same, so is the instruction decoder
- We can save adders by reusing ALU for all the additions
- We have a problem!
We can not perform multiple operation with one component in one cycle.

Big Problem

- Instruction and Data memories can be unified using a multiplexer for the address
- The Instruction and data need to be stored in registers
- Since the instructions are the same, so is the instruction decoder
- We can save adders by reusing ALU for all the additions
- We have a problem!
We can not perform multiple operation with one component in one cycle.
- Therefore we break each instruction into multiple cycles
- The great advantage is that different instructions can have different run of cycles



Fetch

 - Fetch Cycle:
 - The instruction will be fetched from the current PC
 - The fetched instruction will be stored into Instruction Register
 - The current PC will be saved into old PC



Decode

 
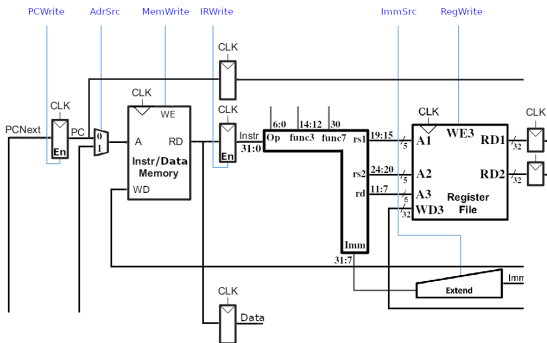
- Decode Cycle:
 - Signals flow combinatorially, no need to issue any control signal



Load Instruction



- MemAdr Cycle:

 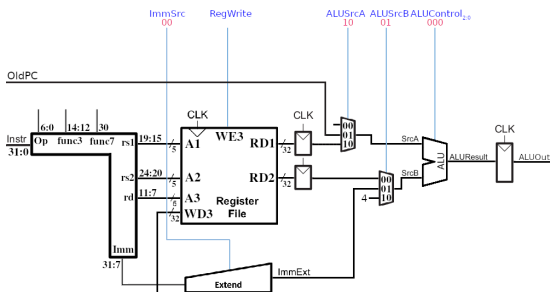- ALU must add the base address and the offset
- The address will be stored in ALUOut register




Load Instruction

 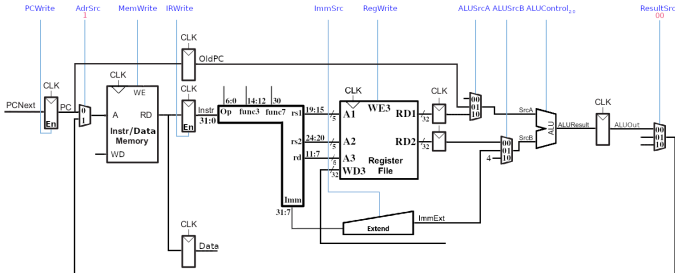- MemRead Cycle:
 - Memory must be read from the address stored in ALUOut
 - The data will be stored in Data register




Load Instruction

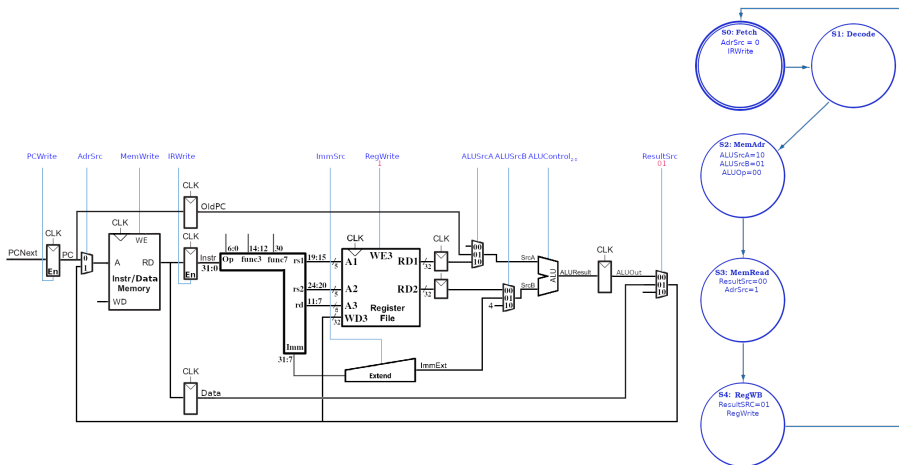- MemWB Cycle:
 - The data stored in Data reg must be written back into register file



Updating PC

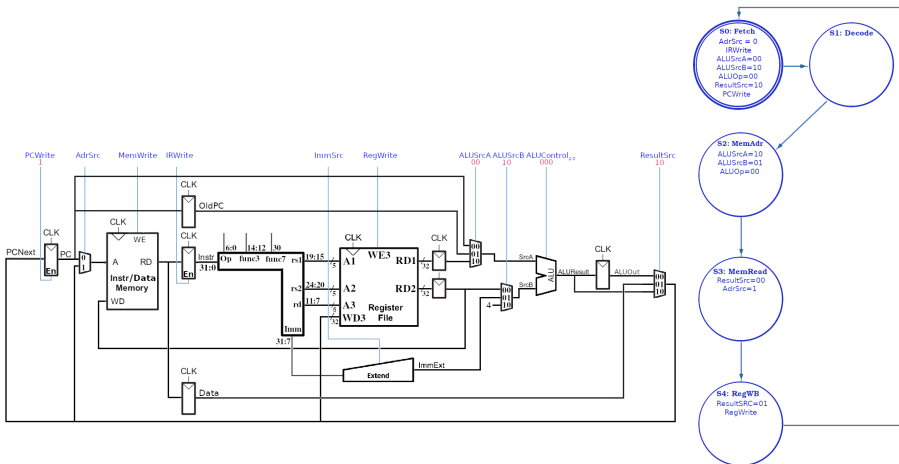
- We increment PC by 4 before fetching the next instruction
- ALU is not being used during Fetch cycle
- We can add necessary control signals to update PC during fetch cycle



Load Instruction

• `lw rd, imm(rs1)`


	PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2,0}	ResultSrc
Fetch:	1	0		1			00	10	000	10

 

Load Instruction

• `lw rd, imm(rs1)`


	PCWrite	AdSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch:	1	0		1			00	10	000	10
Decode:					00					

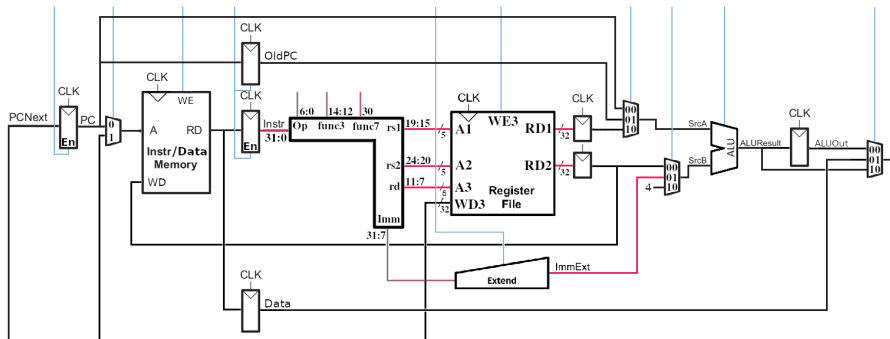

Load Instruction

• `lw rd, imm(rs1)`


	PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch: 1		0		1			00	10	000	10
Decode:					00					
MemAdr:					00		10	01	000	

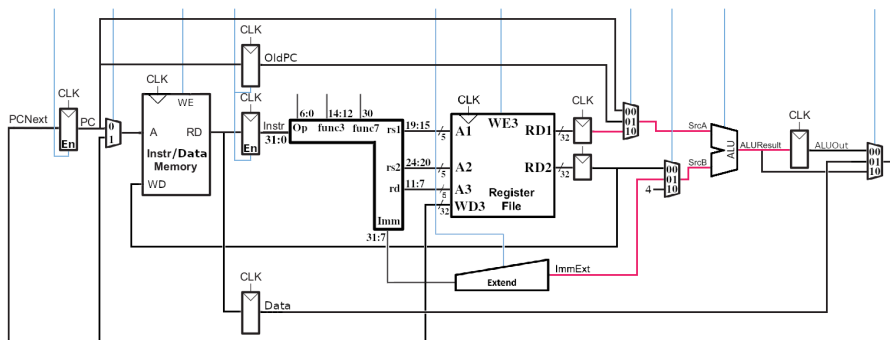

Load Instruction

● `lw rd, imm(rs1)`


	PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl ₂₀	ResultSrc
Fetch:	1	0		1			00	10	000	10
Decode:					00					
MemAdr:					00		10	01	000	
MemRead:		1			00					00

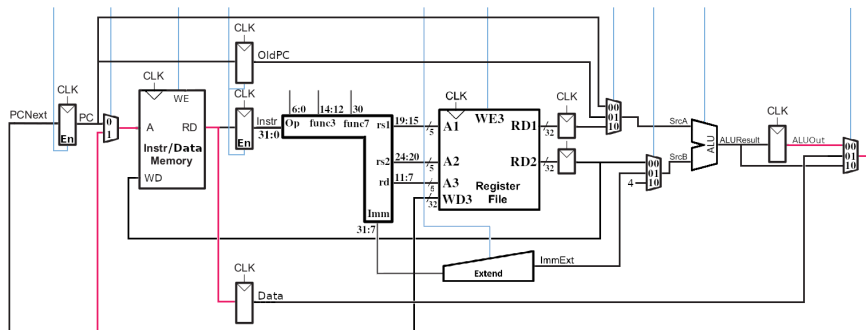

Load Instruction

● `lw rd, imm(rs1)`


	PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl ₂₀	ResultSrc
Fetch:	1	0		1			00	10	000	10
Decode:					00					
MemAdr:					00		10	01	000	
MemRead:		1			00					00
RegWB:					00	1				01

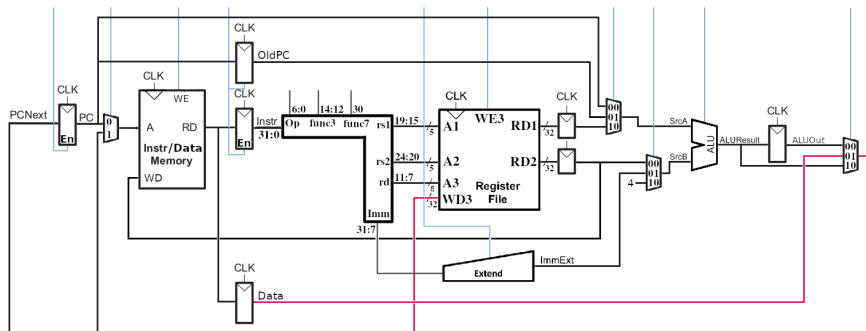

Store Instruction

• `sw rs2, imm(rs1)`


	PCWrite	AdSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2,0}	ResultSrc
Fetch:	1	0		1			00	10	000	10

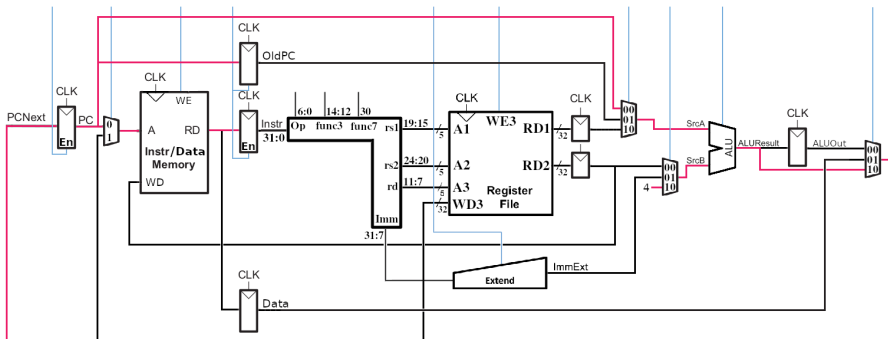

Store Instruction

• `sw rs2, imm(rs1)`


	PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch:	1	0		1			00	10	000	10
Decode:					00					

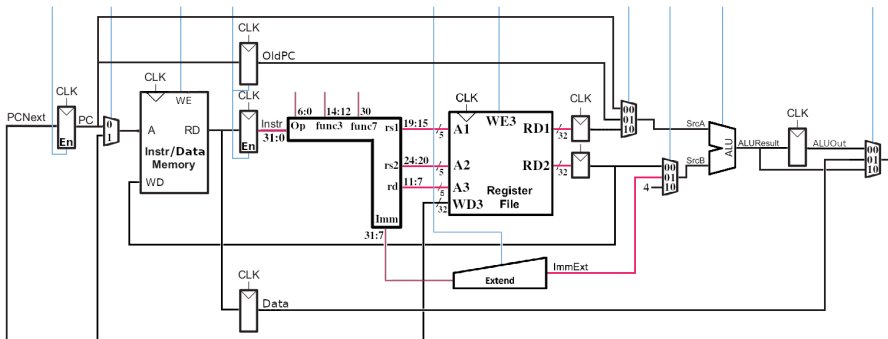

Store Instruction

- `sw rs2, imm(rs1)`


PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch: 1	0		1			00	10	000	10
Decode:				01					
MemAdr:				01		10	01	000	

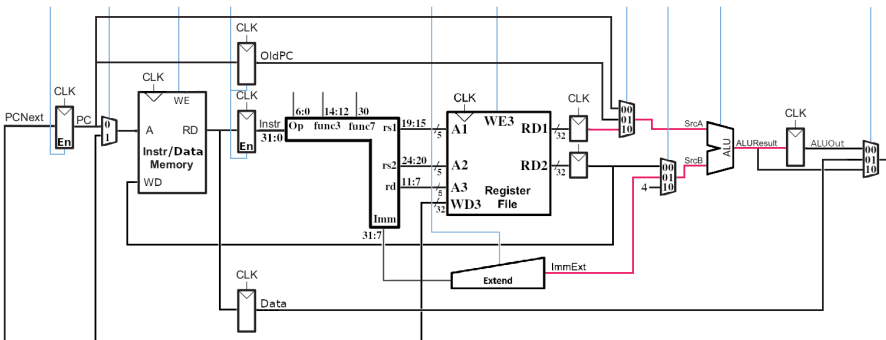

Store Instruction


● `sw rs2, imm(rs1)`

	PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl ₂₀	ResultSrc
Fetch:	1	0		1			00	10	000	10
Decode:					01					
MemAdr:					01		10	01	000	
MemWrite:		1	1							00

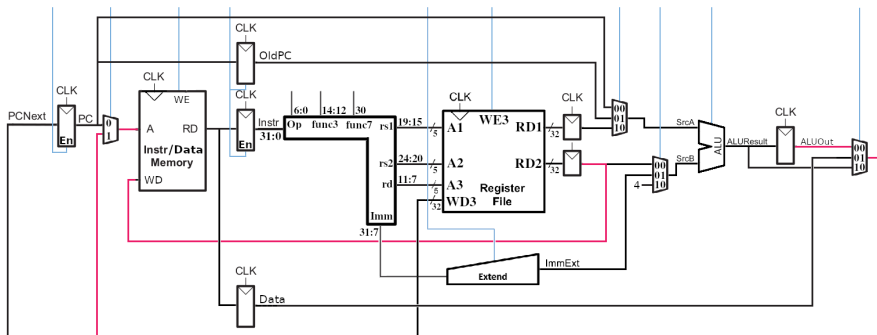

Store Instruction


• `sw rs2, imm(rs1)`

 

R-Type Instruction

• add rd, rs1, rs2


	PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch:	1	0		1			00	10	000	10

 

R-Type Instruction

• add rd, rs1, rs2


	PCWrite	AdrSrc	MemWrite	IRWrite		ImmSrc	RegWrite		ALUSrcA	ALUSrcB	ALUControl _{2:0}		ResultSrc
Fetch:	1	0		1					00	10	000		10
Decode:													

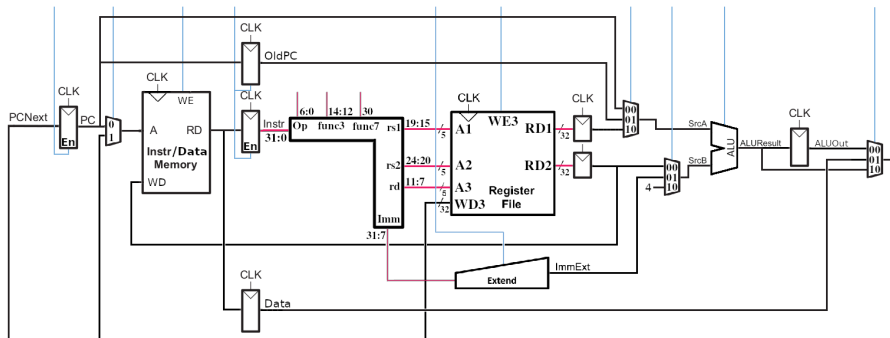

R-Type Instruction

• add rd, rs1, rs2


	PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch: 1		0		1			00	10	000	10
Decode:										
ExecuteR:							10	00	???	

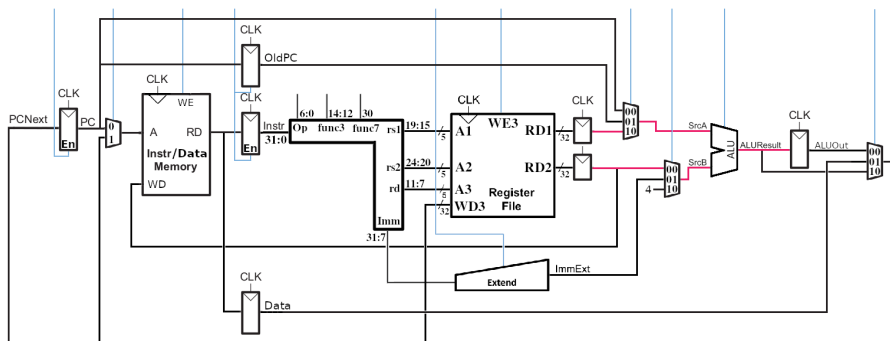

R-Type Instruction


• add rd, rs1, rs2

	PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch: 1		0		1			00	10	000	10
Decode:										
ExecuteR:							10	00	???	
ALUWB:						1				00

 

R-Type Instruction


- `add rd, rs1, rs2`

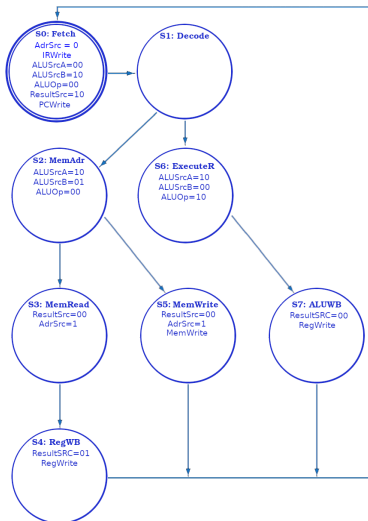

I-Type Instruction

• `addi rd, rs1, imm`


	PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch:	1	0		1			00	10	000	10

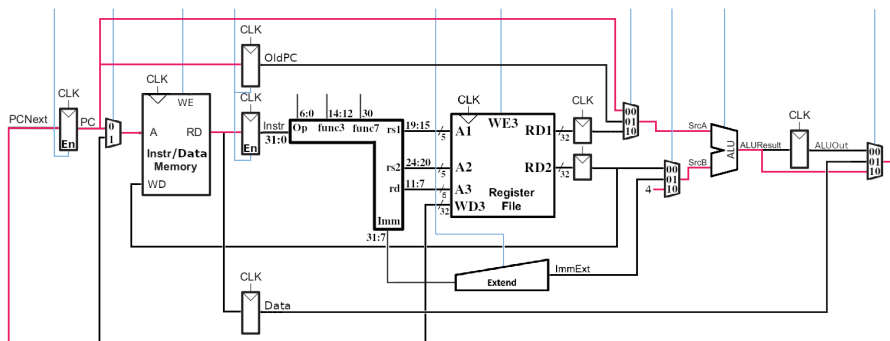

I-Type Instruction

• `addi rd, rs1, imm`


	PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch:	1	0		1			00	10	000	10
Decode:										

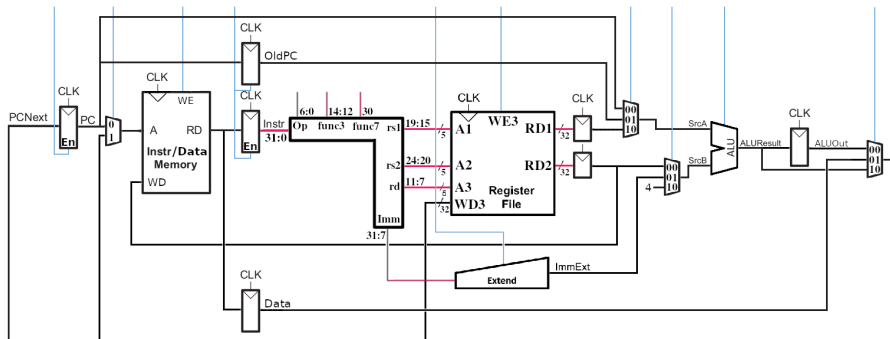

I-Type Instruction

• `addi rd, rs1, imm`


	PCWrite	AdSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch: 1		0		1			00	10	000	10
Decode:										
ExecuteI:							10	01	???	

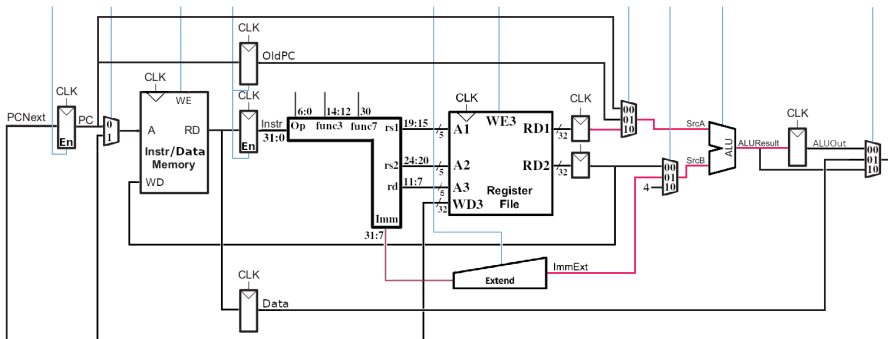

I-Type Instruction


• `addi rd, rs1, imm`

	PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch: 1		0		1			00	10	000	10
Decode:										
Execute I:							10	01	???	
ALUWB:						1				00

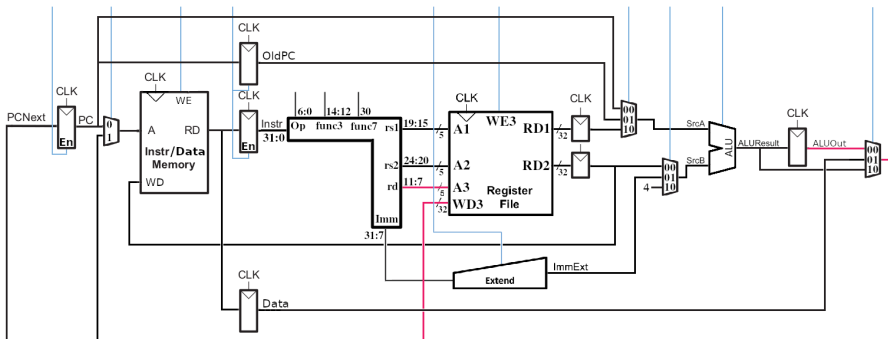

I-Type Instruction


- `addi rd, rs1, imm`

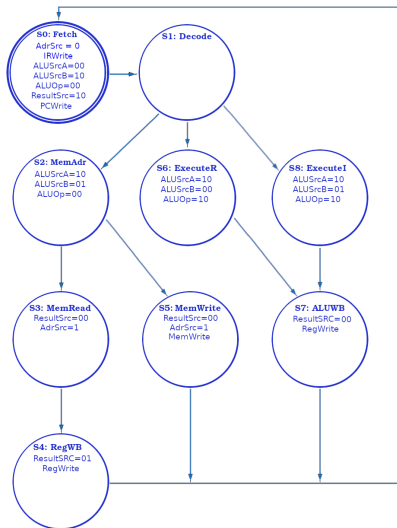

beq Instruction

• beq rs1, rs2, imm


	PCWrite	AdrSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch:	1	0		1			00	10	000	10

 

beq Instruction

• beq rs1, rs2, imm


	PCWrite	AdSrc	MemWrite	IRWrite		ImmSrc	RegWrite		ALUSrcA	ALUSrcB	ALUControl _{2:0}		ResultSrc
Fetch:	1	0		1					00	10	000		10
Decode:						10			01	01	000		

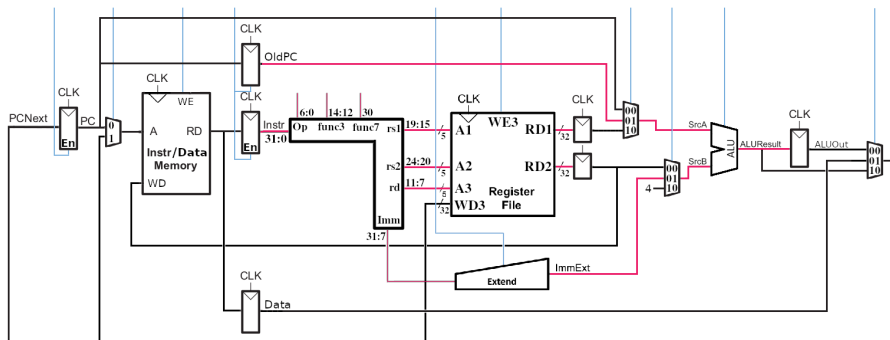

beq Instruction


• beq rs1, rs2, imm

	PCWrite	AdSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch:	1	0		1			00	10	000	10
Decode:					10		01	01	000	
BEQ: Branch & Z							10	00	001	00

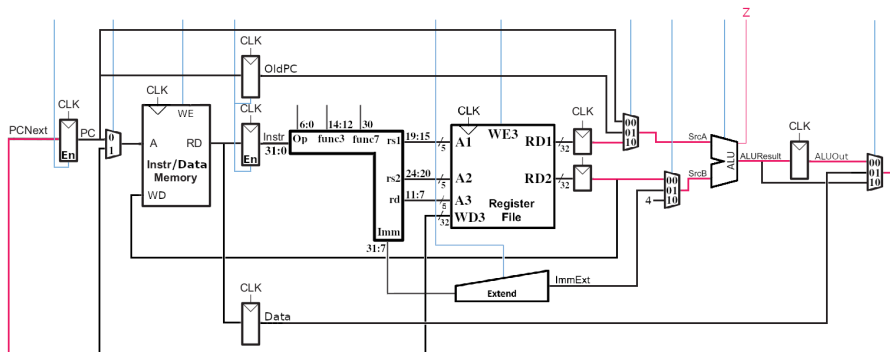

beq Instruction


- beq rs1, rs2, imm

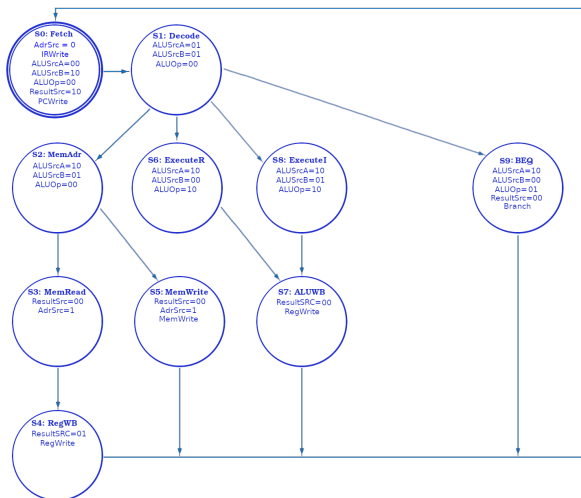

jal Instruction

• `jal rd, imm`


	PCWrite	AdSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch:	1	0		1			00	10	000	10

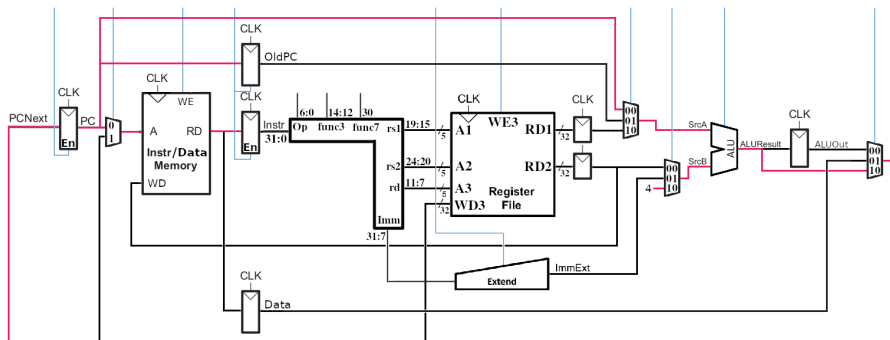

jal Instruction

• `jal rd, label`


	PCWrite	AdSrc	MemWrite	IRWrite		ImmSrc	RegWrite		ALUSrcA	ALUSrcB	ALUControl _{2:0}		ResultSrc
Fetch:	1	0		1					00	10	000		10
Decode:						11			01	01	000		

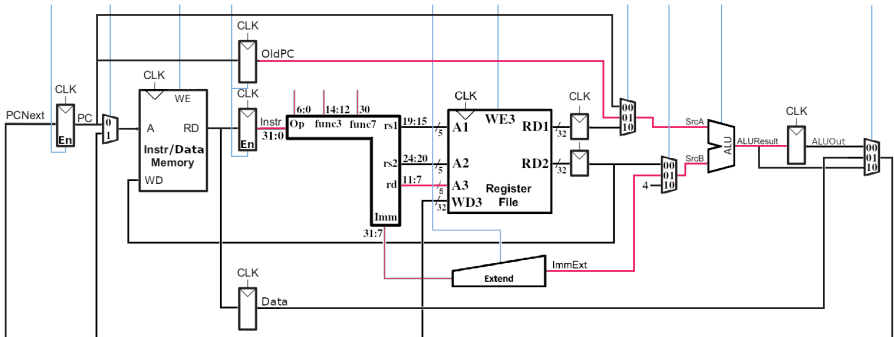

jal Instruction

• `jal rd, label`


	PCWrite	AdSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch: 1		0		1			00	10	000	10
Decode:					11		01	01	000	
JAL: 1							01	10	000	00

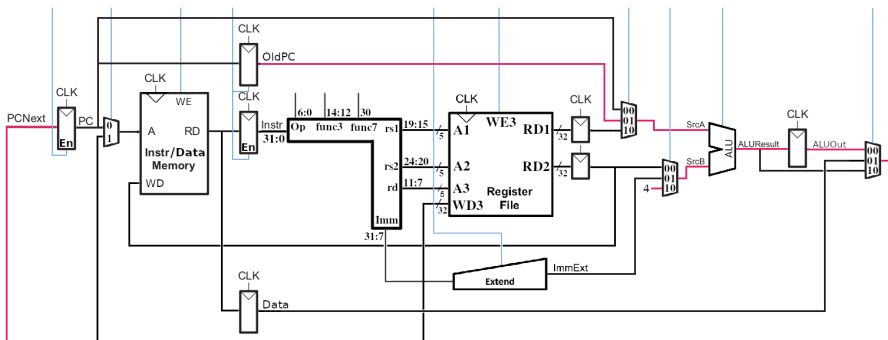

jal Instruction


• `jal rd, label`

	PCWrite	AdSrc	MemWrite	IRWrite	ImmSrc	RegWrite	ALUSrcA	ALUSrcB	ALUControl _{2:0}	ResultSrc
Fetch:	1	0		1			00	10	000	10
Decode:					11		01	01	000	
JAL:	1						01	10	000	00
ALUWB:						1				00

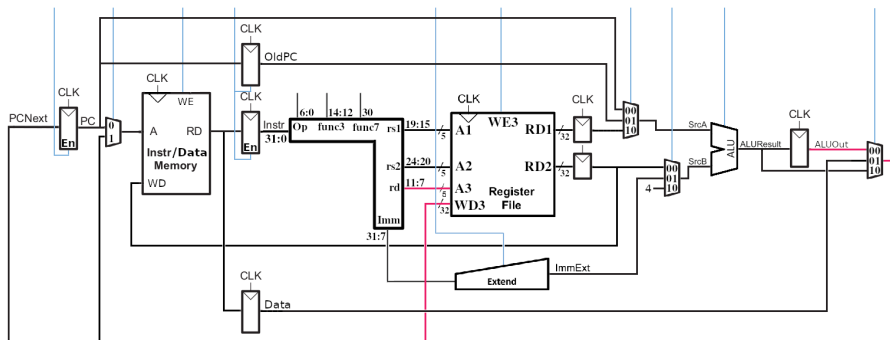

jal Instruction

- `jal rd, label`

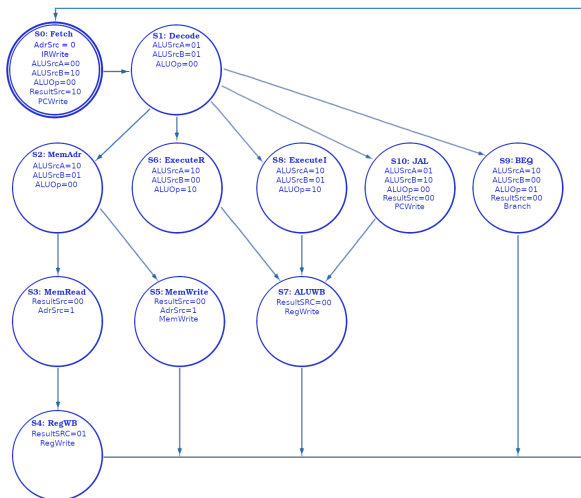


Performance Analysis

- The CPU performance

$$ExecutionTime = (\#Inst.) \times (CPI) \times \frac{1}{F_{clock}}$$

- The cycle time is set by the critical cycle path
- The longest cycle path
 
$$T_{multi} = t_{pcq} + t_{dec} + 2t_{mux} + \max\{t_{mem}, t_{ALU}\} + t_{setup}$$



Performance Analysis

- Given the following delay table,

$$\begin{aligned}
 T_{multi} &= t_{pcq} + t_{dec} + 2t_{mux} + \max\{t_{mem}, t_{ALU}\} + t_{setup} \\
 &= 40 + 25 + 2 \times 30 + 200 + 60 = 385ps
 \end{aligned}$$

Element	Parameter	Delay (ps)
Register clk-to-Q	t_{pcq}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	30
AND-OR gate	t_{AND-OR}	20
ALU	t_{ALU}	120
Decoder (control unit)	t_{dec}	25
Extend unit	t_{ext}	35
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

Performance Analysis

- How long does it take to execution a 100 billion instructions code, if it is composed of 25% Loads, 10% Stores, 11% Branches, 2% Jumps, 52% R- or I-Type instructions?
- According to the state diagram,
 - Load:** 5 cycles
 - Store:** 4 cycles
 - R-Type:** 4 cycles
 - I-Type:** 4 cycles
 - Jump:** 4 cycles
 - Branch:** 3 cycles
- Therefore we can calculate,

$$CPI = 0.25 \times 5 + 0.1 \times 4 + 0.11 \times 3 + 0.02 \times 4 + 0.52 \times 4 = 4.14$$

- Execution time can be calculated as,

$$\begin{aligned}
 ExecutionTime &= (\#Inst.) \times (CPI) \times \frac{1}{F_{clock}} \\
 &= 10^{11} \times 4.14 \times 385 \times 10^{-12} = 159.39 \text{ sec}
 \end{aligned}$$